

Complex Circuits & Electrical Instruments




*"Who wants to hear actors talk?" Harry M.
Warner, Warner Brothers, 1927.*

Complex Circuit


- Complex circuits involve circuit with resistors in Series & Parallel.
- Approach
 1. Find R_{eq} for the entire circuit.
 2. Find current through the battery.
 3. Use Ohm's Law to solve for V or I for different resistors.
 - a) Remember I is constant in series.
 - b) Remember ΔV is constant in parallel.
 - c) Remember voltage must drop to zero after completing the circuit.

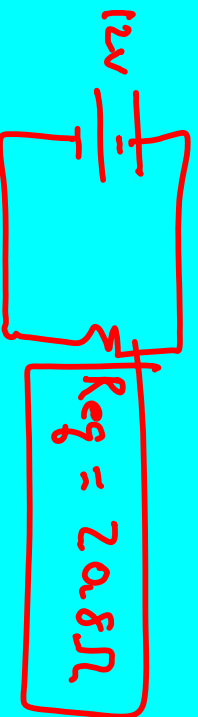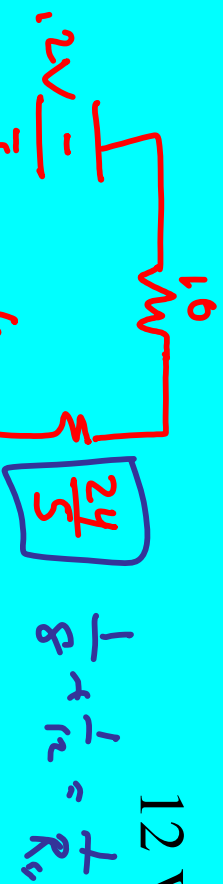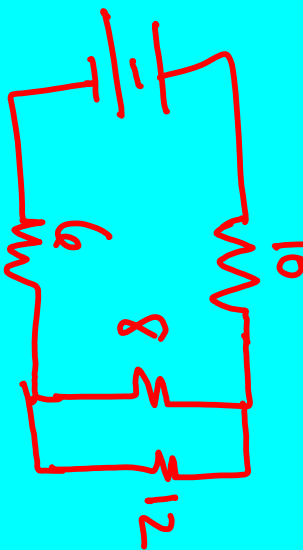Examples

- Find R_{eq} , I through the battery, the voltage drop across the $5\ \Omega$ resistor, and the current through the $8\ \Omega$ resistor.



$12 = I(20.8)$
 $I = .58\ A$

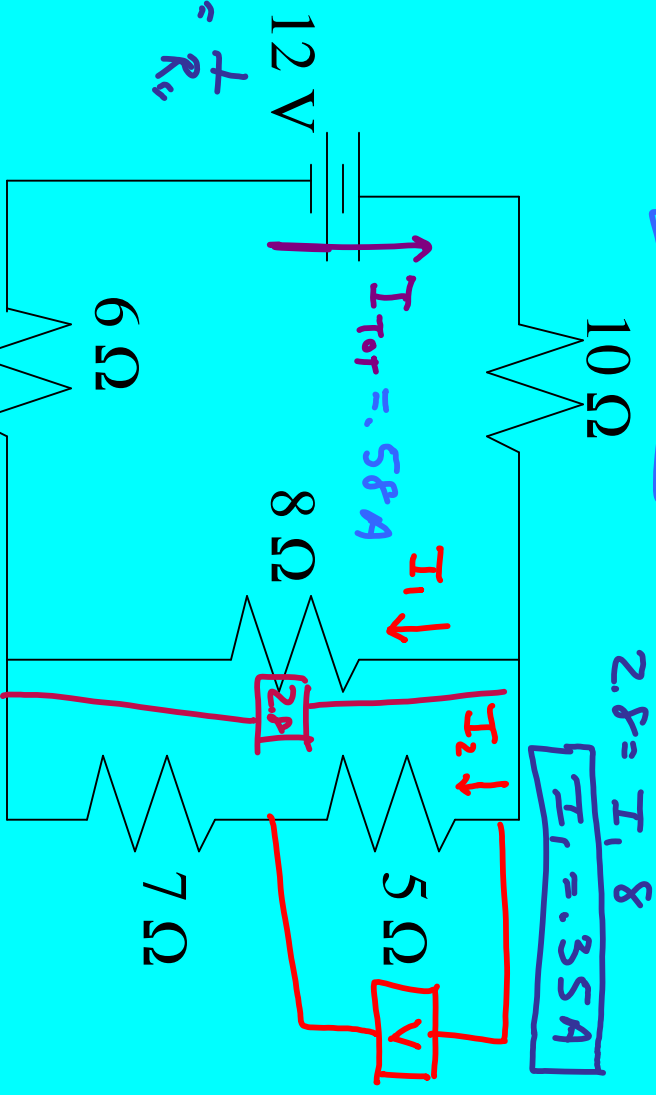

$\Delta V_{11} = .58(\frac{24}{5})$
 $\Delta V_{11} = 2.8\ V$

$2.8 = I_1(8)$
 $I_1 = .35\ A$

$.58 - .35 = I_2 = .23\ A$, $2.8 = I_2(12)$
 $I_2 = .23\ A$

$\Delta V = .23(5) = 1.17\ V$

Electrical Instruments

- A device used to measure current is an ammeter




- How do you connect an ammeter? Series
- What is the resistance of an ideal ammeter?




- A device used to measure potential difference is
Voltmeter

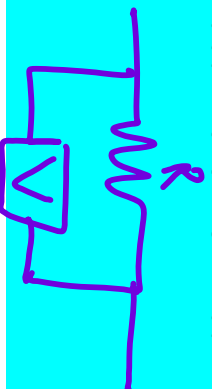- How do you connect a voltmeter? //
- What is the resistance of an ideal voltmeter? ∞





Galvanometer

- The galvanometer is the main component in analog ammeters and voltmeters. Transparency.
- A galvanometer has a resistance of about 60 ohms.
- Is this good for an ammeter? So they connect a ^{Nb} shunt resistor in // with the galvanometer.
- Should the shunt resistor have a high or low resistance?
- To use the galvanometer as a voltmeter, what adjustments should be made.
- Homework questions 38 & 39.

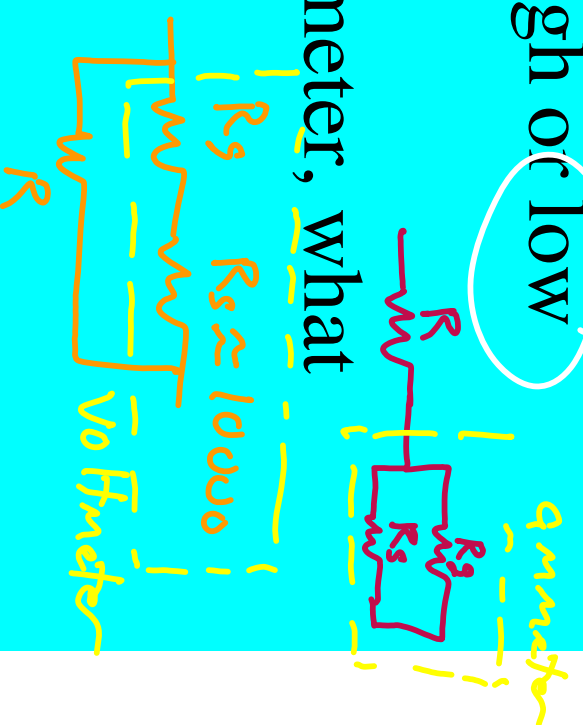

Galvanometer

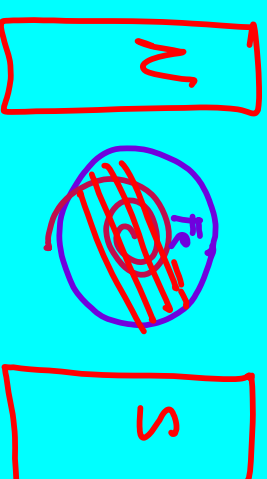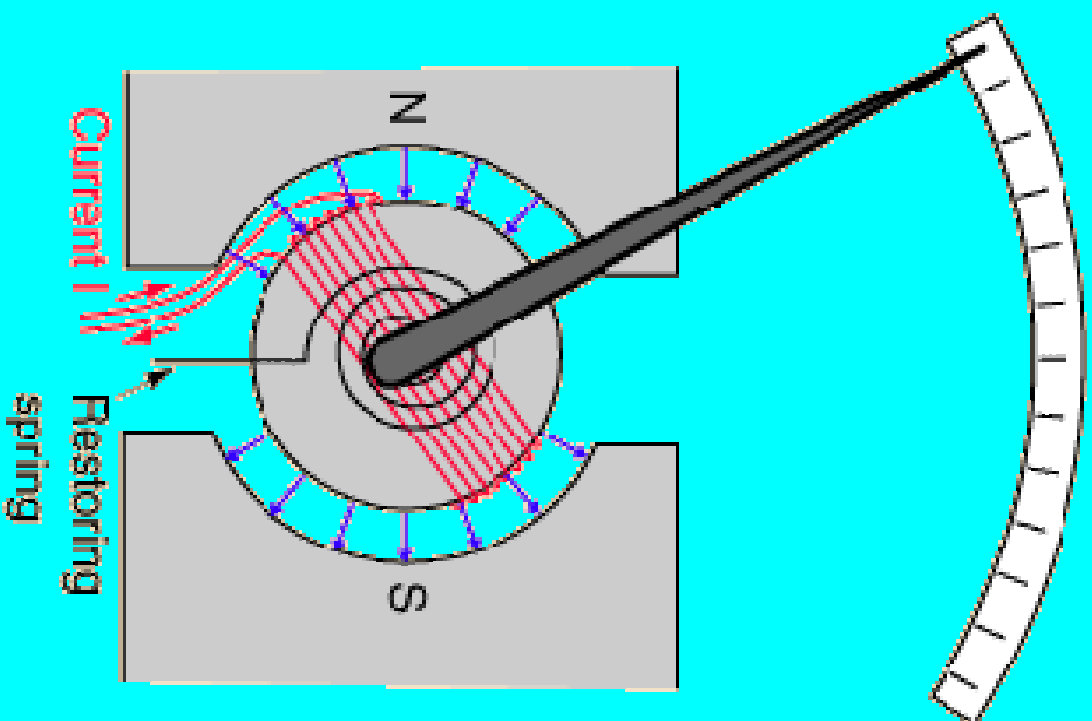

Wheatstone Bridge

- An unknown resistor can be measured using a wheatstone bridge.
- The circuit is balanced when no current flows through the galvanometer.

- Solve for R_x


$$V_a = V_b$$

$$R_1 I_1 = R_2 I_2$$

$$R_2 I_1 = R_x I_2$$

$$R_x = \frac{R_2 R_3}{R_1}$$

→
variable resistor
(potentiometer)

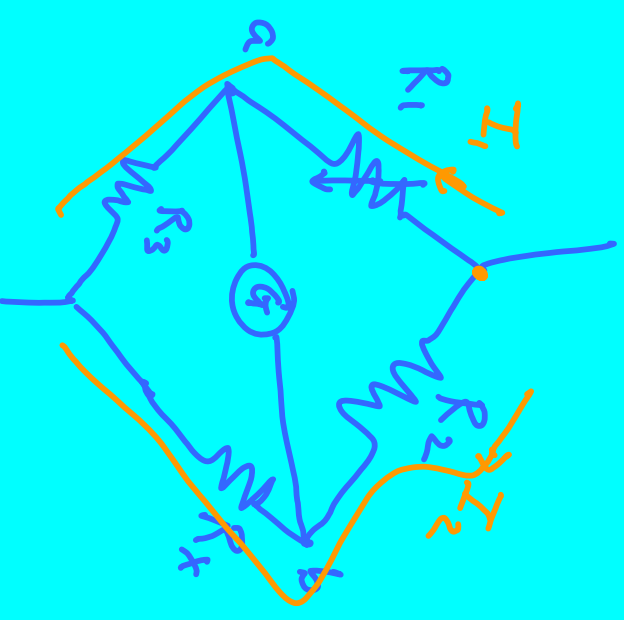

- A potentiometer is a variable resistor.