

## RC Circuits

"The concept is interesting and well-formed, but in order to earn better than a 'C,' the idea must be feasible." A Yale University management professor in response to Fred Smith's paper proposing

reliable overnight delivery service. (Smith went on to found Federal Express Corp.)

# RC Circuits

$$\Delta V = IR$$
$$C = \frac{Q}{\Delta V}$$

- Draw a schematic of an RC circuit, and apply Kirchoff's loop rule to the circuit. Assume the

capacitors starts uncharged.

$$\Sigma - IR - \frac{Q}{C} = 0$$



- The maximum current through the circuit is given

by

$$I_{\text{MAX}} = \frac{\epsilon}{R} @ t=0$$

- The maximum charge on each plate is given by

$$Q_{\text{MAX}} = C \epsilon @ t=\infty$$

# Charging the Capacitor

- Write a differential equation for the circuit and solve

for  $q(t)$  and  $I(t)$ .

$$\left( \frac{E - \frac{dq}{dt}}{R} - \frac{q}{C} = 0 \right) R$$

$$\frac{E}{R} - \frac{q}{RC} = \frac{dq}{dt}$$

$$\frac{E_C - q}{RC} = \frac{dq}{dt}$$

$$-\int_0^t \frac{dt}{RC} = \int_0^q \frac{dq}{E_C - q}$$

$$-\frac{t}{RC} = \ln \left( \frac{q}{E_C - q} \right) \Big|_0^q$$

$$-\frac{t}{RC} = \ln \left( \frac{q_i - E_C}{q_i} \right)$$

$$-\frac{t}{RC} = \ln \left( \frac{q_i - E_C}{-E_C} \right)$$

$$e^{-\frac{t}{RC}} = \frac{q_i - E_C}{-E_C}$$

$$\boxed{q_i(t) = E_C \left( 1 - e^{-\frac{t}{RC}} \right)}$$


$$q(\infty) = Q_{\max} = E_C$$

$$\boxed{I(t) = \frac{dq}{dt} = E_C \left( +e^{-\frac{t}{RC}} \right) \left( \frac{1}{RC} \right)}$$

$$\boxed{I(t) = \frac{E}{R} e^{-\frac{t}{RC}}}$$

$$I(0) = I_{\max} = \frac{E}{R}$$

$$I(\infty) = 0$$

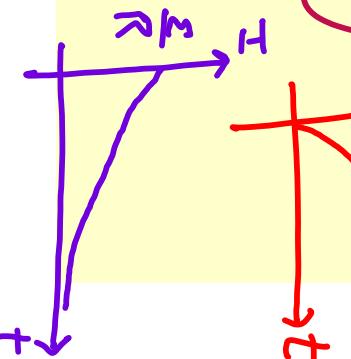


time constant:  $\tau = RC$ , time for  $I_0$  decrease to  $\frac{1}{e} I_0$

## Discharging a Capacitor

- Consider a capacitor carrying an initial charge,  $Q_0$ , connected to a resistor,  $R$ , and a switch. Write a differential equation for the circuit and solve for  $q(t)$  and  $I(t)$ .

$$\left( \frac{\frac{q}{C} - IR}{R} = 0 \right) \downarrow R$$

$$I = -\frac{dq}{dt}$$

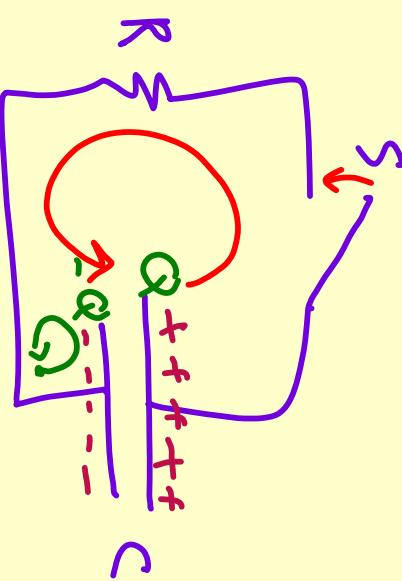

$$\int_{0}^{t_1} \frac{-\frac{dq}{dt}}{RC} dt = \int_{Q_0}^{Q_1} \frac{dq}{C}$$

$$-\frac{t_1}{RC} = \ln \frac{Q_1}{Q_0}$$

$$-\frac{t_1}{RC} = \ln \left( \frac{Q_1}{Q_0} \right)$$

$$e^{-\frac{t}{RC}} = \frac{Q_1}{Q_0}$$

$$Q e^{-\frac{t}{RC}} = Q_0$$

$$I(t) = \frac{-\frac{dq}{dt}}{RC} = \frac{Q_0}{RC} e^{-\frac{t}{RC}}$$

# Example


1. An uncharged capacitor is connected in a circuit as shown below.

$$I = \frac{E}{R} e^{-\frac{t}{\tau}}$$

$$\tau = \frac{E}{I} = \frac{E}{\frac{E}{R}} = R$$

$$e^{-1} = \frac{1}{e}$$

$t = \tau = RC$

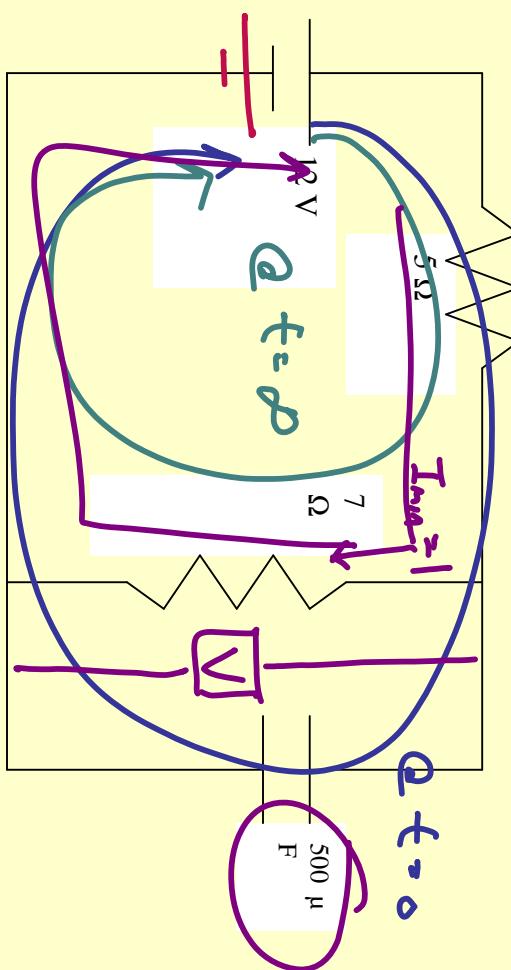


- a) Find the time constant of the circuit  $\tau = RC = 5 (500 \times 10^{-6}) = 0.025s$
- b) Find the maximum current in the circuit. @  $t=0$   $I_{max} = \frac{12}{7} = 2.4A$
- c) Find the minimum current in the circuit.  $I_{min} = \frac{12}{12} = 1A$
- d) Find the maximum charge on the capacitor.
- e) Graph the current through each resistor vs. time.

$$d) C = \frac{Q}{\Delta V} \Rightarrow Q = C \Delta V$$

$$\Delta V = 1(\text{V}) = 7 \text{ V across } \parallel \text{ branch}$$
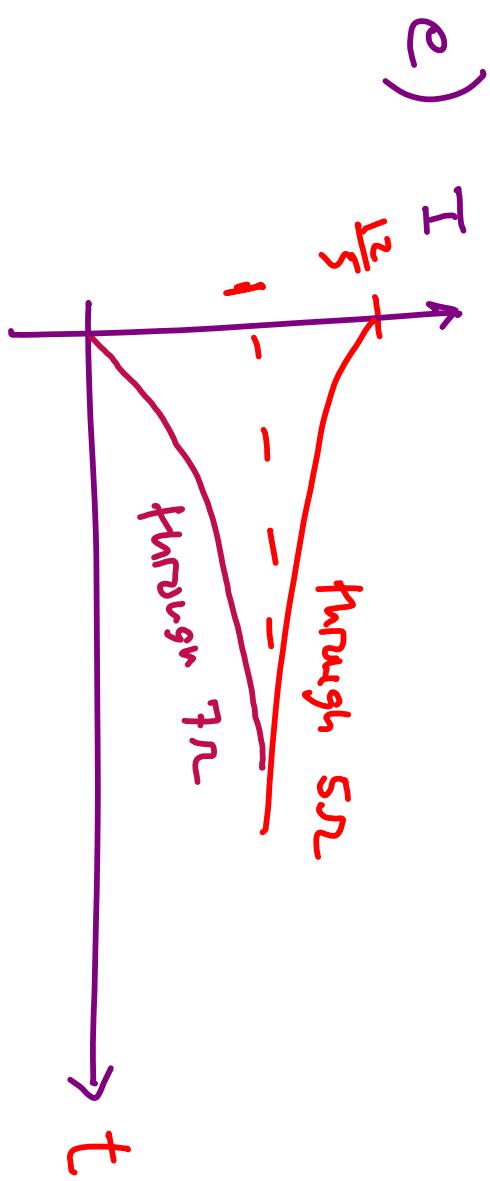
$$Q = 7(500 \times 10^{-6}) = .0035 \text{ C}$$



A game C.I.