

Combinations of Capacitors

"Computers in the future may weigh no more than 15 tons." --
Popular Mechanics, forecasting
the relentless march of science,
1949.



Parallel Capacitors

- ★ Symbols for battery, capacitor, switch.
- ★ Draw capacitors in parallel.
- ★ How does potential difference across the two capacitors compare?


- ★ Solve for C_{eq} .

$$C = \frac{Q}{\Delta V}$$

$$Q_{TOT} = Q_1 + Q_2$$

$$C_{eq} \Delta V = C_1 \Delta V + C_2 \Delta V$$
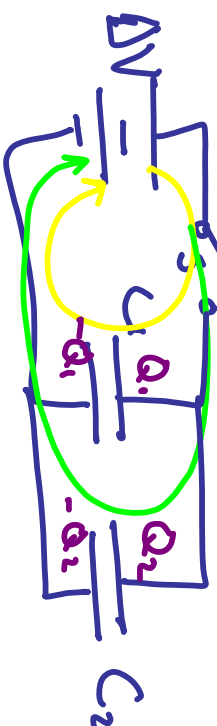
$$C_{eq} = C_1 + C_2 + \dots \text{ for } \parallel$$



$$\Delta V = \frac{Q}{C}$$



$$Q_{TOT} = C_{eq} \Delta V$$




Series Capacitors

- ★ Draw capacitors in series and label charge on each plate.
- ★ How does charge on each plate compare? *equal*

- ★ Solve for C_{eq} .

$$C = \frac{Q}{\Delta V}$$

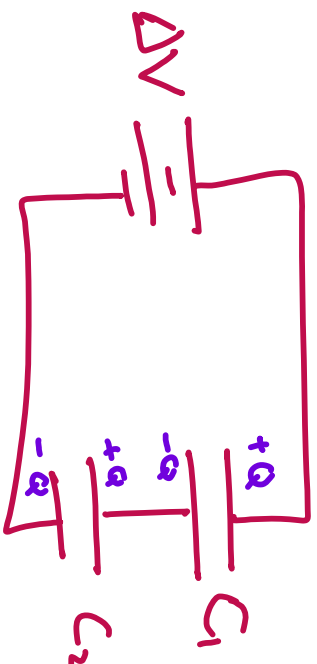

$$\Delta V = \Delta V_1 + \Delta V_2$$

$$\frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \sum \frac{1}{C_i}$$

Series



Problem Solving




1. Find C_{eq} for the circuit.
2. Find charge stored by ΔV . *Q_{net}*
3. Then determine Q or ΔV on each capacitor by doing C_{eq} in reverse, and remembering whether Q or ΔV is constant for each.

Example: $C_1 = 12 \mu\text{F}$, $C_2 = 5.3 \mu\text{F}$,

$C_3 = 4.5 \mu\text{F}$, & $\Delta V = 12.5 \text{ V}$

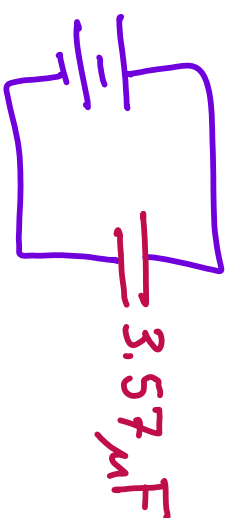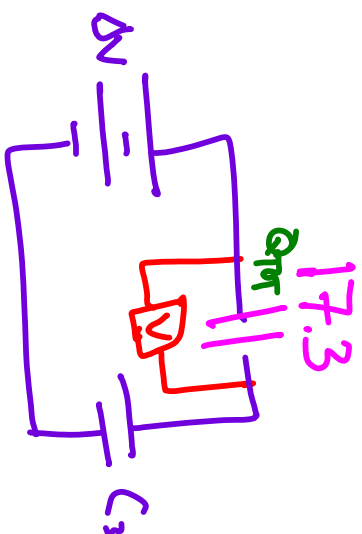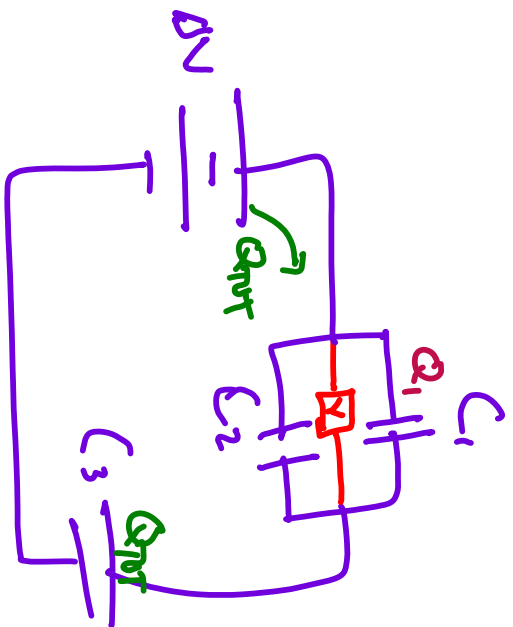- a) Find C_{eq} . *$= 3.57 \mu\text{C}$*
- b) Find charge on C_1 .





$$\frac{1}{17.3} + \frac{1}{4.5} = \frac{1}{C_{eq}}$$


$$C = \frac{Q}{\Delta V} \Rightarrow 3.57 = \frac{Q}{12.5} \Rightarrow Q_{out} = 44.6 \mu C$$

$$17.3 = \frac{44.6}{\Delta V} \Rightarrow \Delta V = 2.58 V$$

$$C = \frac{Q}{\Delta V} \Rightarrow 12 = \frac{Q}{2.58} \Rightarrow Q = 31 \mu C$$

FR III #2 & #3

$P = BR$

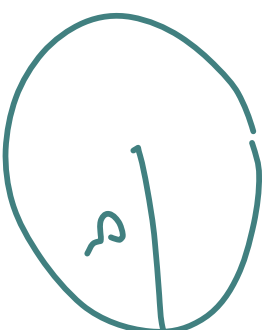

#2 $\frac{d\phi}{dt} =$

(A) Bombs density

i. ii.

(B) $Q = \rho \pi a^4 \leq \text{Show}$

$$\frac{dq}{dV} = \rho$$

$$\int dq = \int \rho dV$$

$$Q = \int_0^a \rho r (4\pi r^2 dr)$$

$$4\pi \rho \frac{r^4}{4} \Big|_0^a = \boxed{\pi \rho a^4}$$

(C)