

Energy, Mutual Inductance & Oscillations in LC Circuits


"640k ought to be enough for anybody." -- Bill Gates,
1981

If you cannot explain what you did, then the
doing has not been worth it. *Heisenberg*

Time is a great teacher, but unfortunately it kills
all its pupils. *Berlioz*

Not everything that counts can be counted, and not
everything that can be counted counts. (Sign
hanging in Einstein's office at Princeton)

Energy

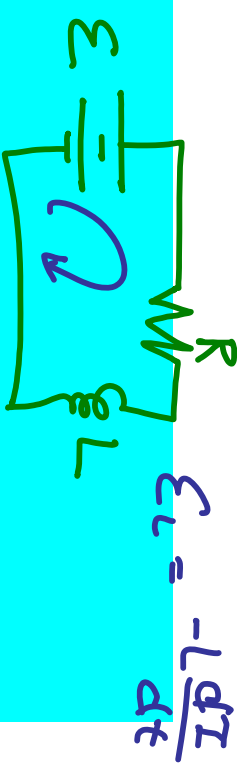

- Draw a LR circuit with a battery and write the differential equation for the loop.

$$\left(\mathcal{E} - IR - L \frac{dI}{dt} = 0 \right) I$$

- Multiply the equation by I to get

$$I \mathcal{E} = I^2 R + LI \frac{dI}{dt}$$

$$P_{\text{battery}} = P_{\text{resistor}} + P_{\text{inductor}}$$

- This equation is an example of conservation of energy


$$P_L = \int \frac{dU_L}{dt} = \int LI \frac{dI}{dt}$$

$$U_L = \frac{1}{2} LI^2$$

- Solve for U_L .

Mutual Inductance

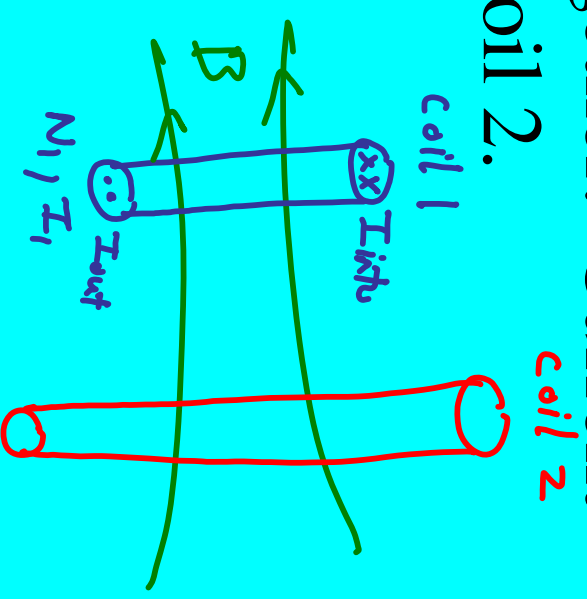- Consider two coils that are close together. Current in coil 1 will create a flux through coil 2.



- We define mutual inductance as

$$M_{12} = \frac{N_2 \Phi_{12}}{I_1} \text{ of coil 2 w.r.t. coil 1}$$

- Solve for the *emf* induced in coil 2


$$\mathcal{E}_2 = -N_2 \frac{d\Phi_{12}}{dt} = -N_2 \frac{d}{dt} \left(\frac{M_{12} I_1}{N_1} \right) \quad \Phi_{12} \text{ - flux through coil 1}$$

$$\mathcal{E}_2 = M_{12} \frac{dI_1}{dt}, \quad \mathcal{E}_1 = -M_{21} \frac{dI_2}{dt}$$

- In mutual inductance, the *emf* induced in one coil is always proportional to the rate at which the current in the other coil is changing.

Oscillations in LC Circuits

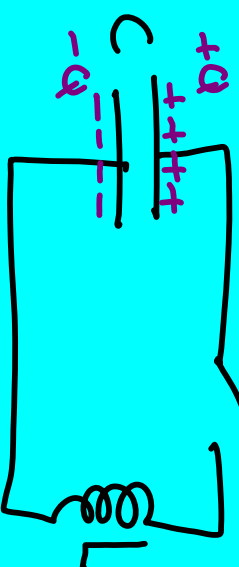- Draw an LC circuit with a switch and a charged capacitor.



- We will assume no energy lost by internal energy (which implies R is zero) or radiation.
- Use transparency to discuss energy transfer.

- Start with the initial energy and solve for ω .

$$U_{\text{tot}} = U_C + U_L$$

$$U = \frac{Q^2}{2C} + \frac{LI^2}{2}$$

$$\frac{dU}{dt} = \frac{Q}{C} \frac{dQ}{dt} + LI \frac{dI}{dt} = 0$$

$$\cancel{\frac{Q}{C}} + LI \cancel{\frac{dI}{dt}} = 0$$

$$L \frac{dI}{dt} = -\frac{Q}{C}$$

$$\frac{d^2Q}{dt^2} = -\frac{1}{LC} Q$$

$$\frac{d^2x}{dt^2} = -\omega^2 x$$

$$\omega^2 = \frac{1}{LC}$$

$$q(t) = Q_{\text{max}} \cos \omega t$$

$$I(t) = -Q \omega \sin \omega t$$

RLC Oscillations



- Draw an RLC circuit with a charge capacitor.

- Use Kirchoff's Rules to derive a differential equation.


$$L \frac{d^2q}{dt^2} + IR + \frac{q}{C} = 0$$

$$m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = 0$$

L → inertia
R → dampening

- Compare this to a spring/mass system with a $C \rightarrow$ restoring force
- resistive force due to dampening.

- Draw the graph of the oscillation.

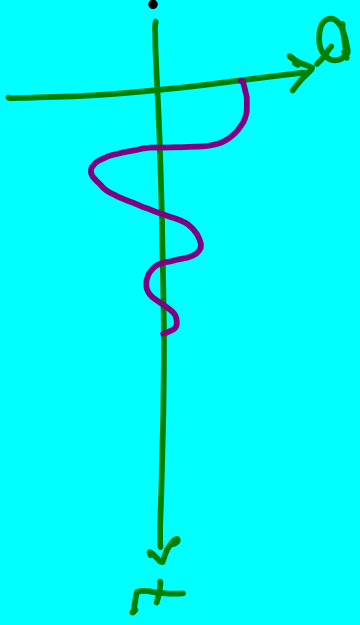

- Why doesn't capacitor just discharge until neutral?