

RL Circuits

A mathematician is a machine for turning coffee into theorems. Erdos

Inductors

coils (solenoids) with a large self-inductance

- What is an inductor?
- An inductor always opposes the changes in the current through the circuit.
- Draw an RL circuit with a switch.



$$\mathcal{E}_L = -L \frac{dI}{dt}$$

- Use Kirchhoff's voltage law to get a differential equation.

$$\mathcal{E} - L \frac{dI}{dt} - IR = 0$$

$$\frac{dI}{dt} > 0 \Rightarrow \mathcal{E}_L < 0$$

Solution

- Derive the solution to the RL circuit.

$$\mathcal{E} - IR = L \frac{dI}{dt}$$

$$\int_0^{t_1} dt = L \int_0^{I_1} \frac{dI}{\mathcal{E} - IR}$$

$$t_1 = -\frac{L}{R} \ln(\mathcal{E} - IR) \Big|_0^{I_1}$$


$$-\frac{Rt_1}{L} = \ln\left(\frac{\mathcal{E} - IR}{\mathcal{E}}\right)$$

$$e^{-\frac{Rt_1}{L}} = \frac{\mathcal{E} - IR}{\mathcal{E}}$$

$$\boxed{\frac{\mathcal{E}}{R} (1 - e^{-\frac{Rt}{L}}) = I}$$

$e^{-\frac{t}{\tau}}$

$\tau = \frac{L}{R}$ for LR circuits

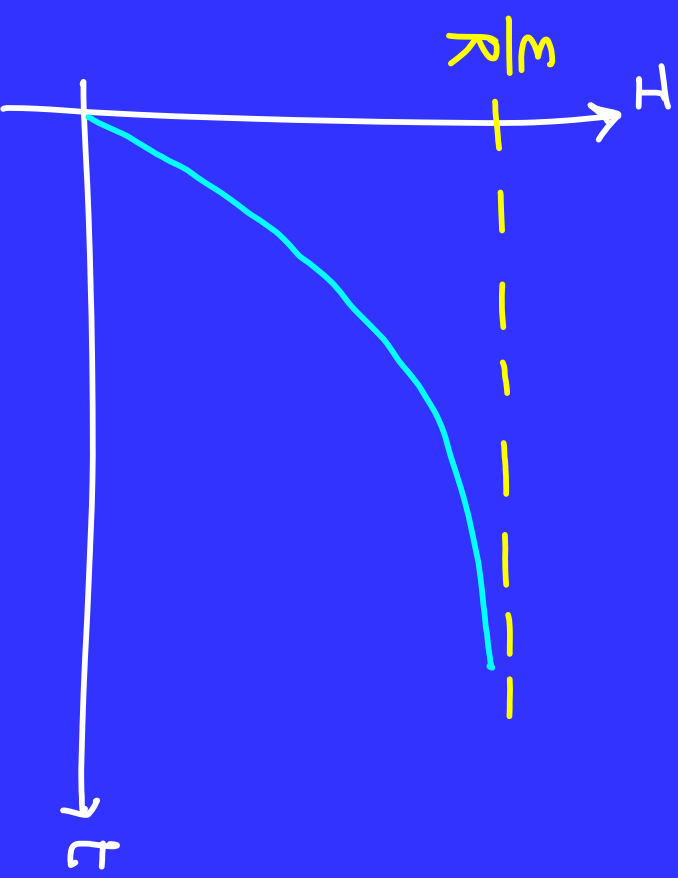

$$\int \frac{dI}{-RI} = -\frac{1}{R} \ln(-RI)$$

Example

- Copy the circuit diagram, and describe changes in the circuit when the switches are opened/closed.



close S_1 : I increases to $\frac{\mathcal{E}}{R}$ as shown before
 close S_2 & open S_1 simultaneously:

$$A: -IR + L \frac{dI}{dt} = 0$$


$$\frac{dI}{dt} < 0 \Rightarrow \mathcal{E} > 0$$

$$L \frac{dI}{dt} = -IR \Rightarrow \int_{I_0}^{I_1} \frac{dI}{I} = -\frac{R}{L} \int_0^{t_1} dt$$

$$\ln\left(\frac{I_1}{I_0}\right) = -\frac{R}{L} t_1$$

$$I_1 = I_0 e^{-\frac{R}{L} t_1}$$

opposing battery

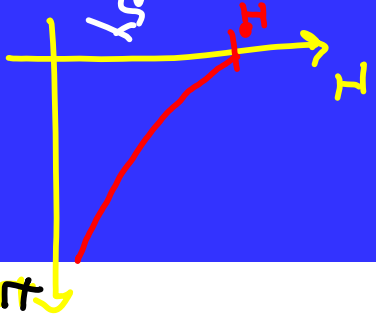

- $\Delta V_L = -L \frac{dI}{dt}$
- At $t = 0$, an inductor acts like an opposing battery.
- At $t = \infty$, and inductor acts like a wire.

Examples

1. Two circuits similar to the previous example have different inductors. Switch 1 is closed at $t = 0$ and then switch 2 is closed. Copy the graphs shown. Which circuit has the greater inductor?
2. A 12 V battery is in series with a 30 mH inductor and a 6 ohm resistor.
 - a) How long does it take the current to reach $2(1 - e^{-1})$ amps?
 - b) Calculate the current at 2 ms.
 - c) Sketch the voltage across the inductor and the resistor.


1. R is same

$L_B > L_A$

$\tau_B > \tau_A$

$\tau = \frac{L}{R}$

$L_B > L_A$

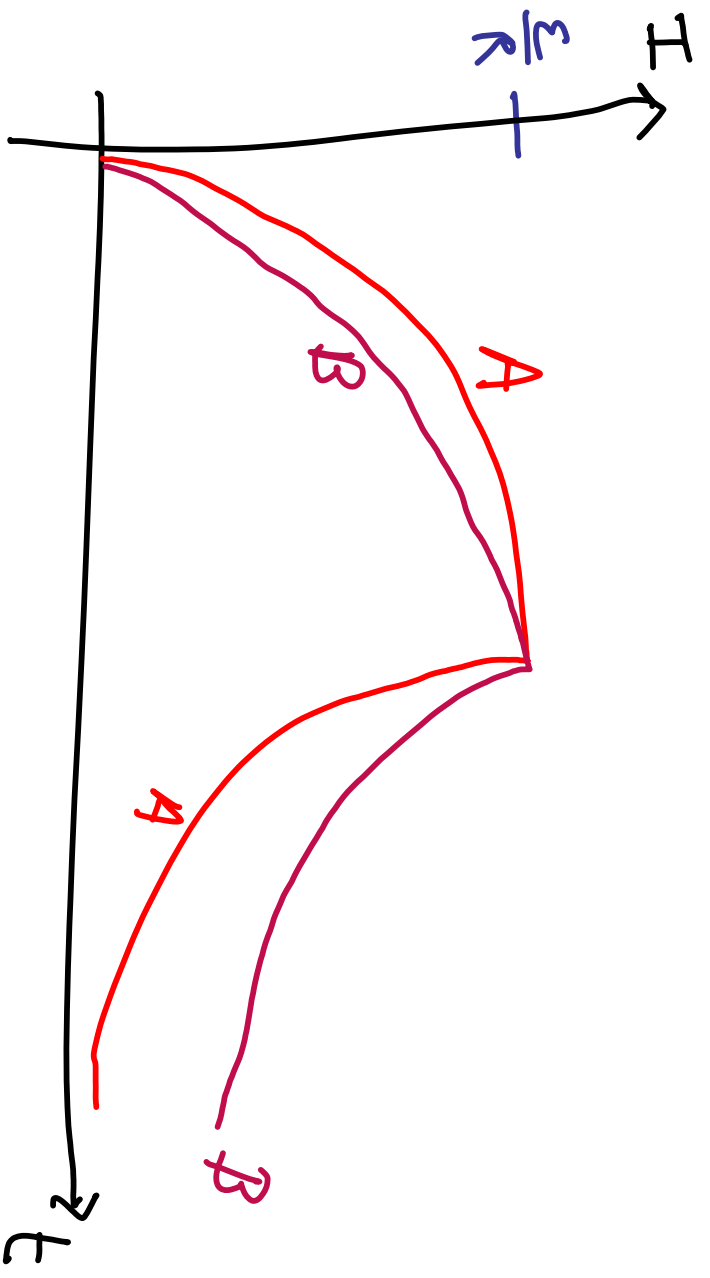

2. (a) $I = 2(1 - e^{-t})$ takes how long?

$$I = \frac{E}{R}(1 - e^{-\frac{t}{\tau}})$$

$$I = 2(1 - e^{-\frac{t}{\tau}})$$

$$\tau = \frac{L}{R} = \frac{30}{6} = 5 \text{ ms}$$

(b) $I = 2(1 - e^{-\frac{t}{5}}) = 0.66 \text{ A}$

(c)

